


Name : Rahul Bhadane

Roll no: 23104B0003

EXPERIMENT 2


Aim: Implementing and simulating basic current mirror circuit using 180nm NMOS TX.

Circuit Diagram:

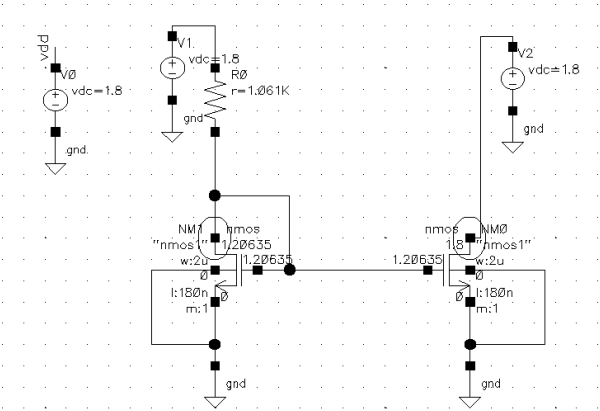


Results:


1mA

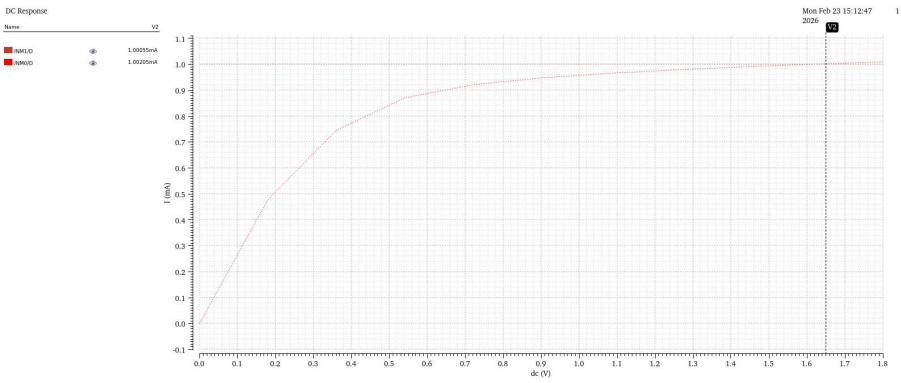

2mA

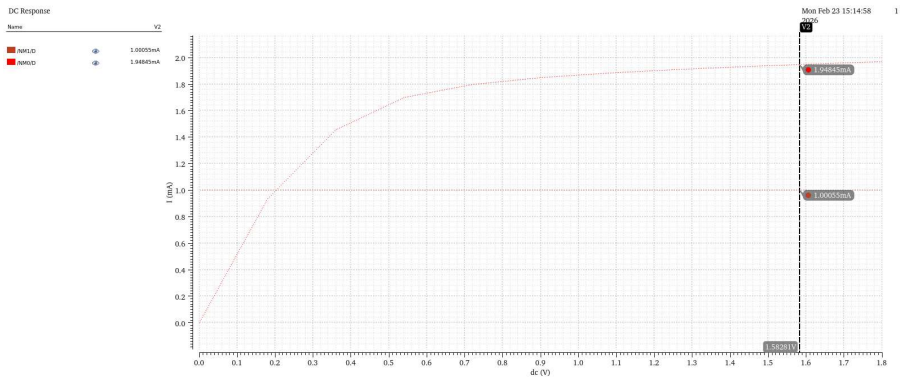

0.5mA

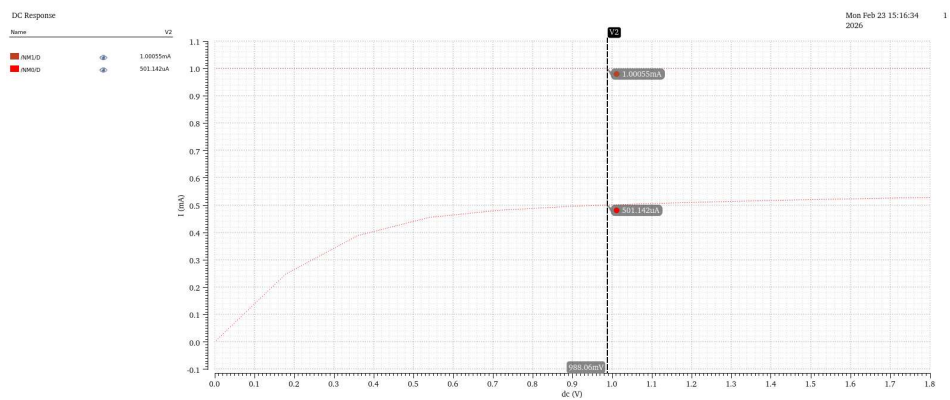

Conclusion: The basic current mirror circuit using a 180 nm NMOS transistor was successfully implemented and simulated. The results showed that the output current closely follows the reference current, validating the principle of current mirroring. This experiment helped in understanding device matching, biasing conditions, and the effect of transistor parameters on current accuracy.