


Name : Rahul Bhadane

Roll No: 23104B0003


EXPERIMENT 4

Aim : Analog Layout of CMOS Inverter

Layout:

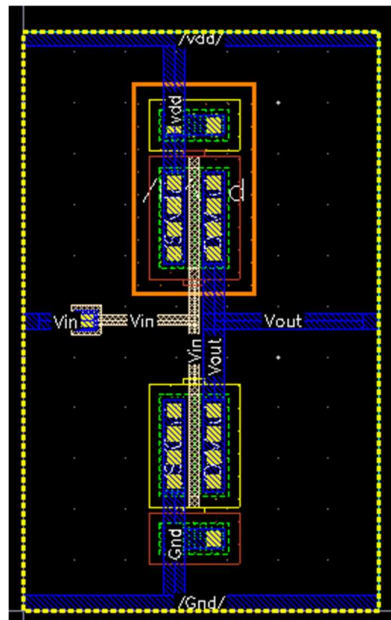

DRC:

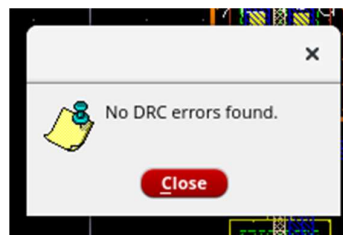

LVS:

