


Name : Rahul Bhadane

Roll no :23104B0003

LAB EXPERIMENT 6

Aim :Design of Bandgap reference

Circuit:

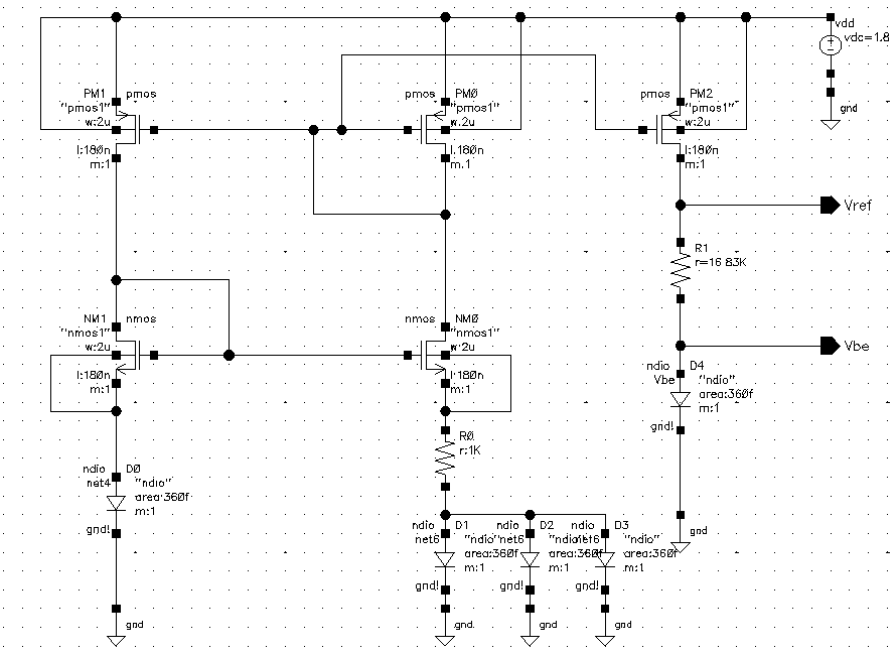

Result:

