


Name : Rahul Bhadane

Roll No : 23104B0003

AICD LAB EXPERIMENT 7


Aim : Design and Simulation of Differential Amplifier

Circuit:

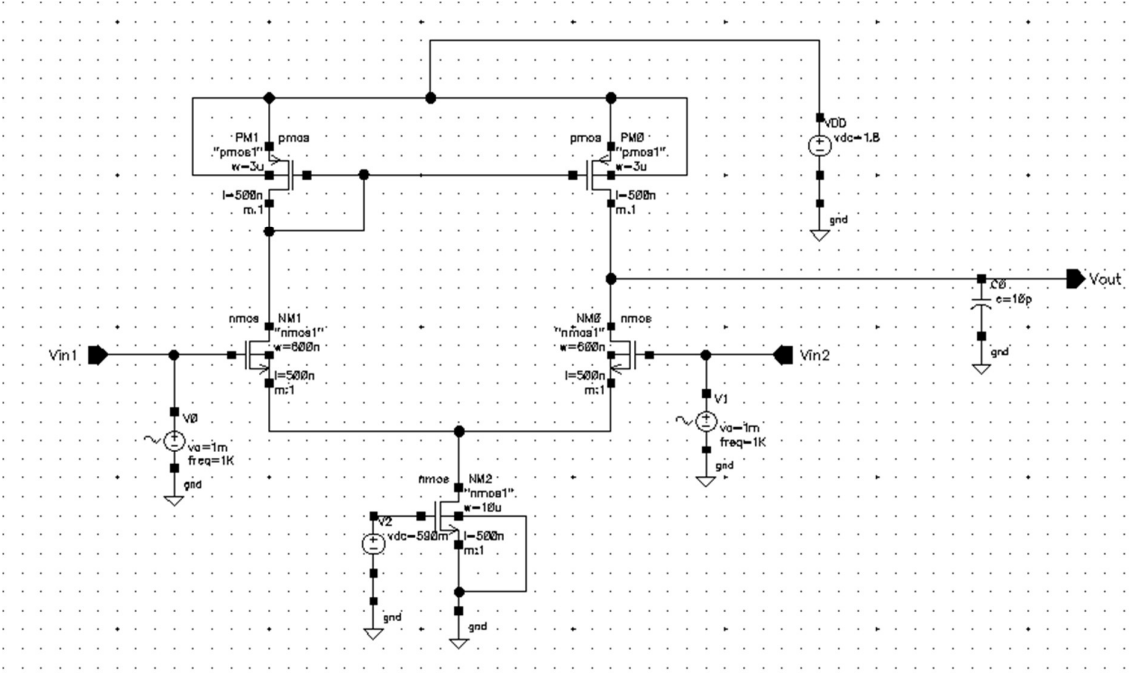


Results:

DC ANALYSIS

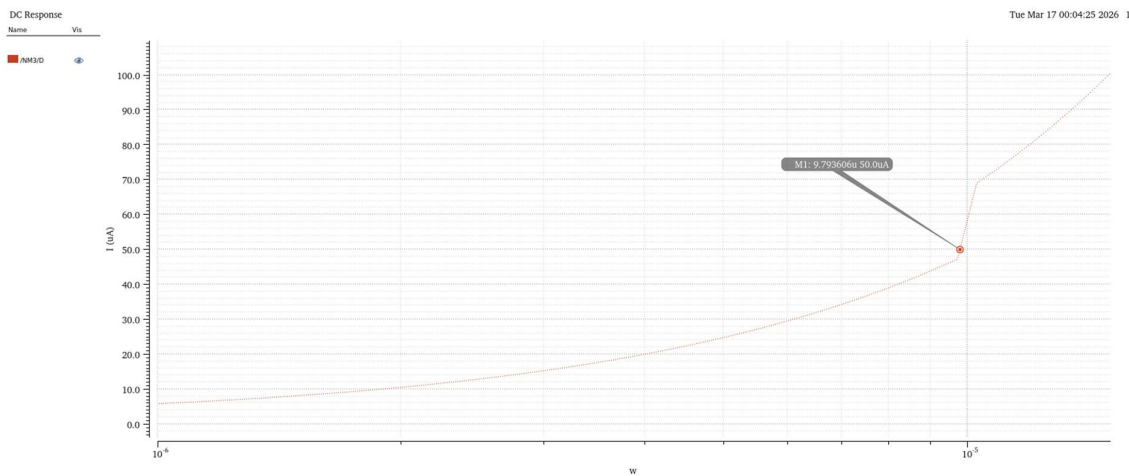

AC ANALYSIS

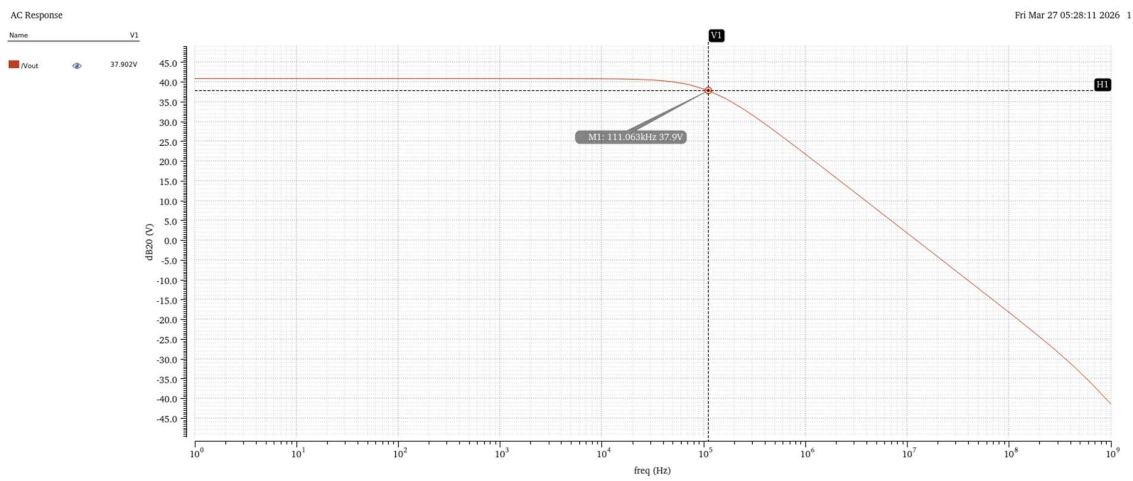

TRANSIENT ANALYSIS

