


Name : Rahul Bhadane

Roll No : 23104B0003

AICD EXPERIMENT 8


Aim: Design of Differential Amplifier

Circuit Diagram:

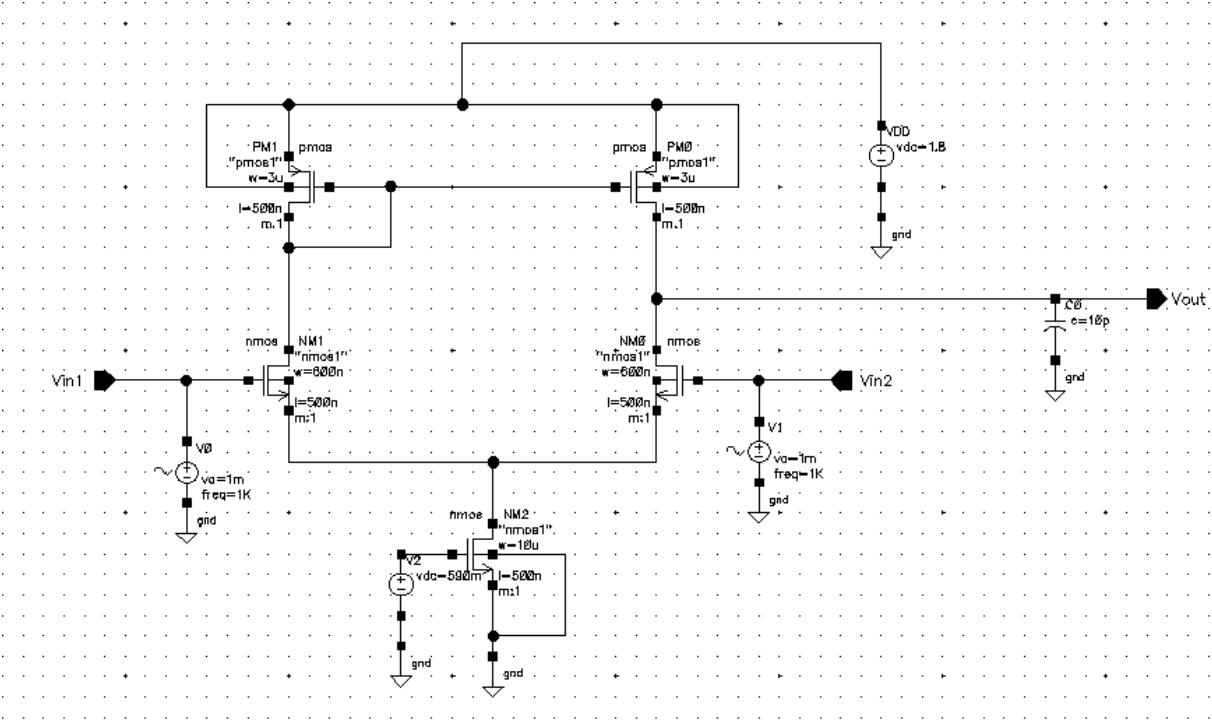


Analysis:


DC Analysis:

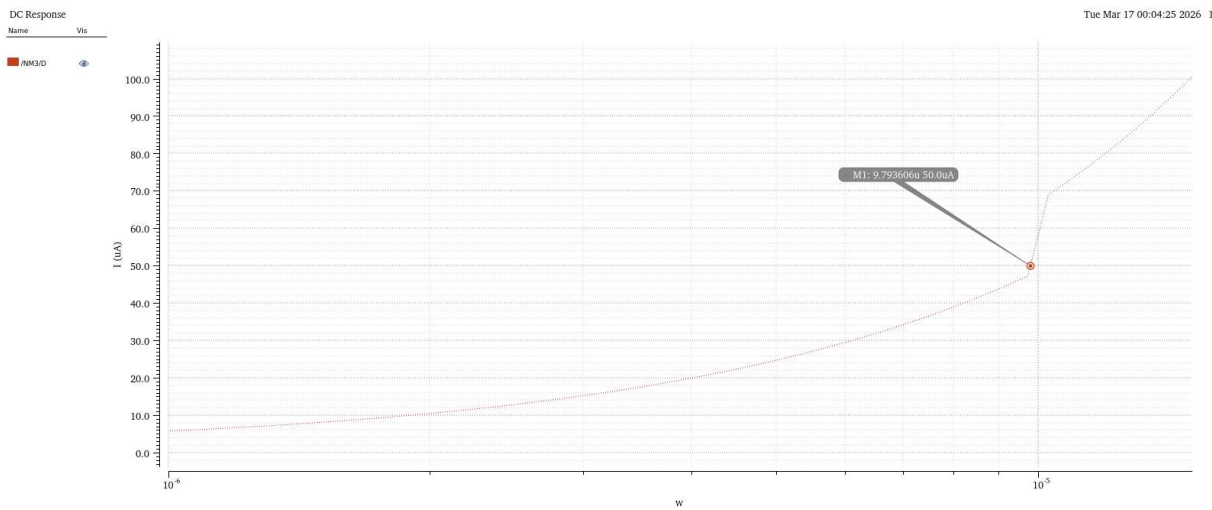

AC Analysis:

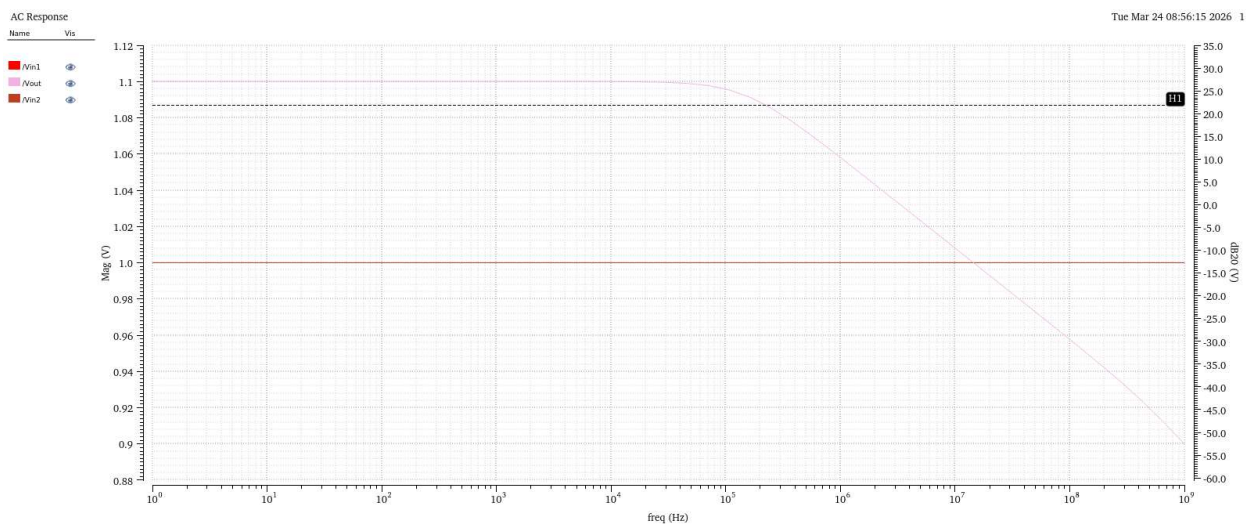

Transient Analysis:

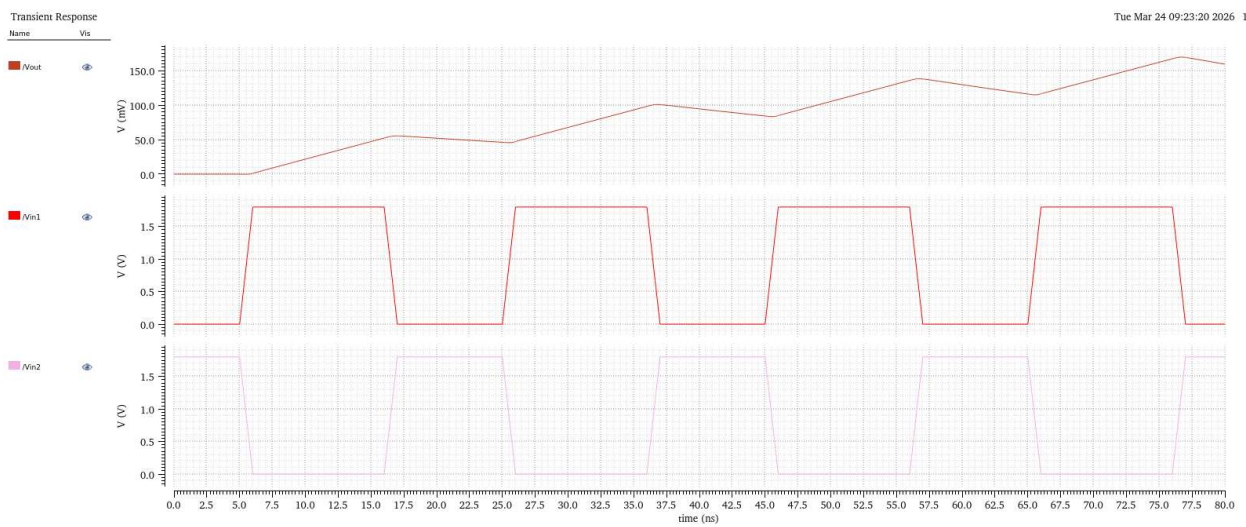

Conclusion:

The differential amplifier is able to amplify the difference between two input signals while rejecting common signals, making it useful in many analog circuits.