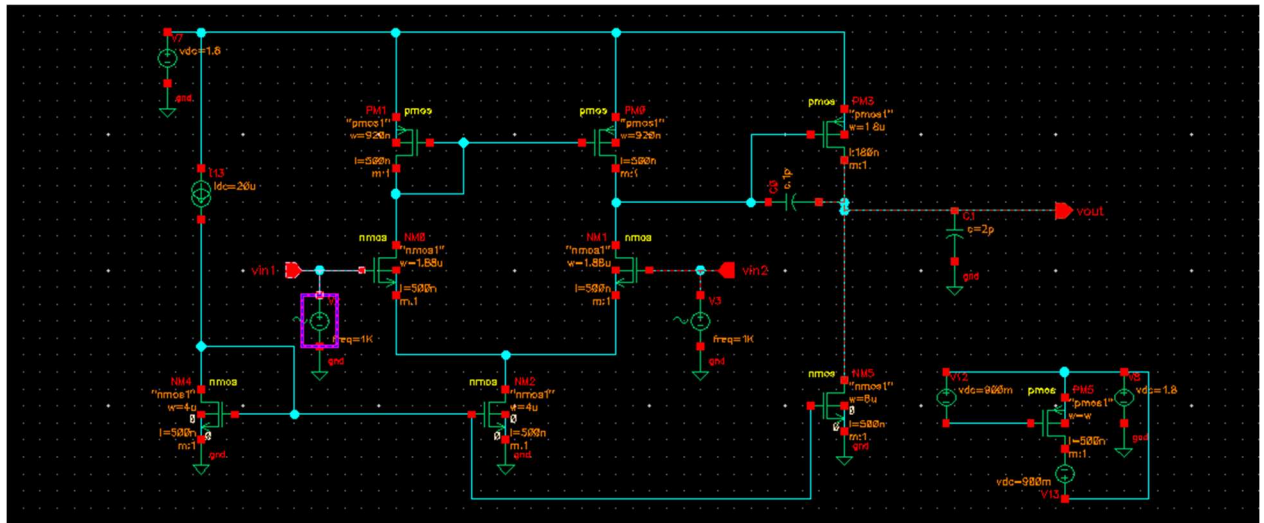


Roll No : 23104B0003


AICD EXPERIMENT 9

Aim: Design of 2 staged operational amplifier


Diagram:



AC Analysis:

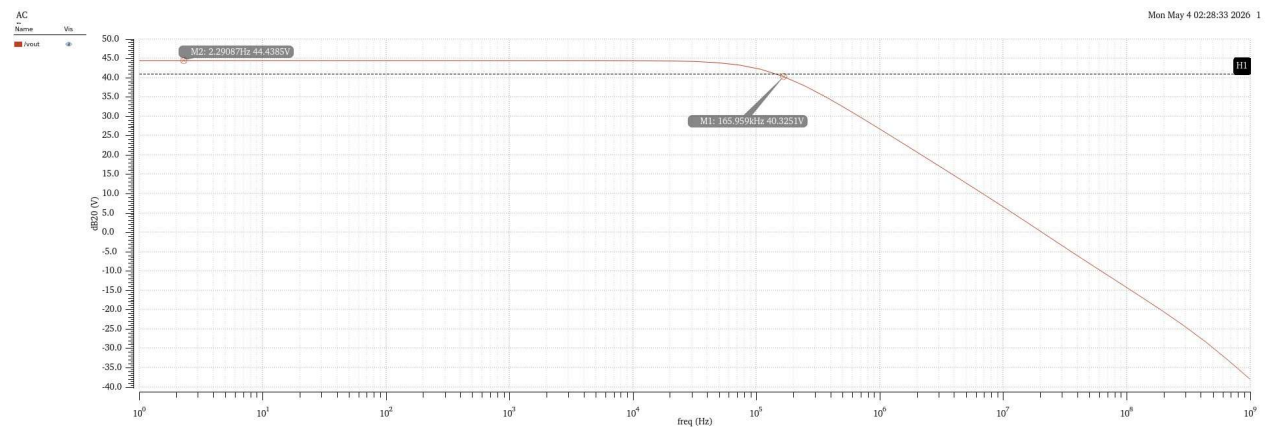

Transient Analysis:

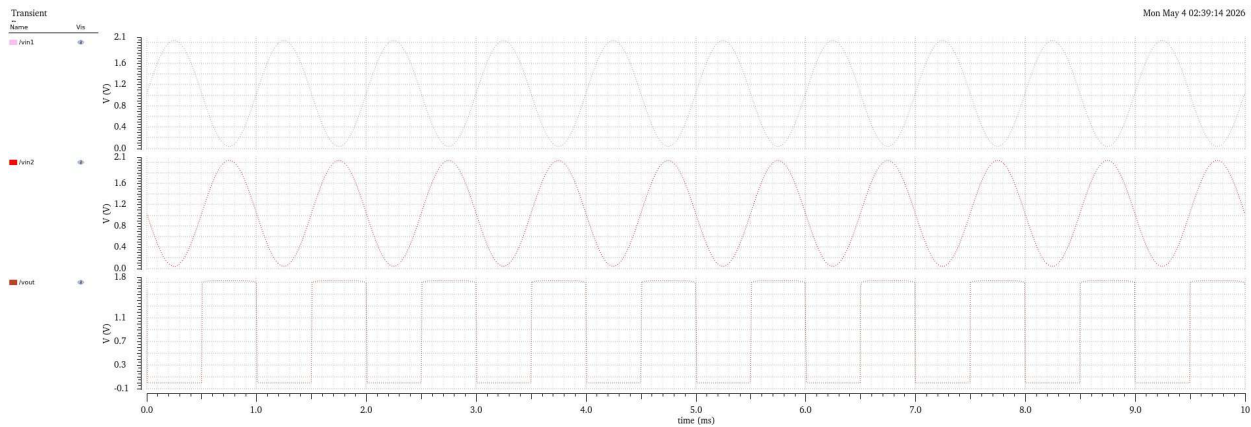

Conclusion: A two-stage operational amplifier provides high voltage gain by combining a differential input stage with a gain/output stage.