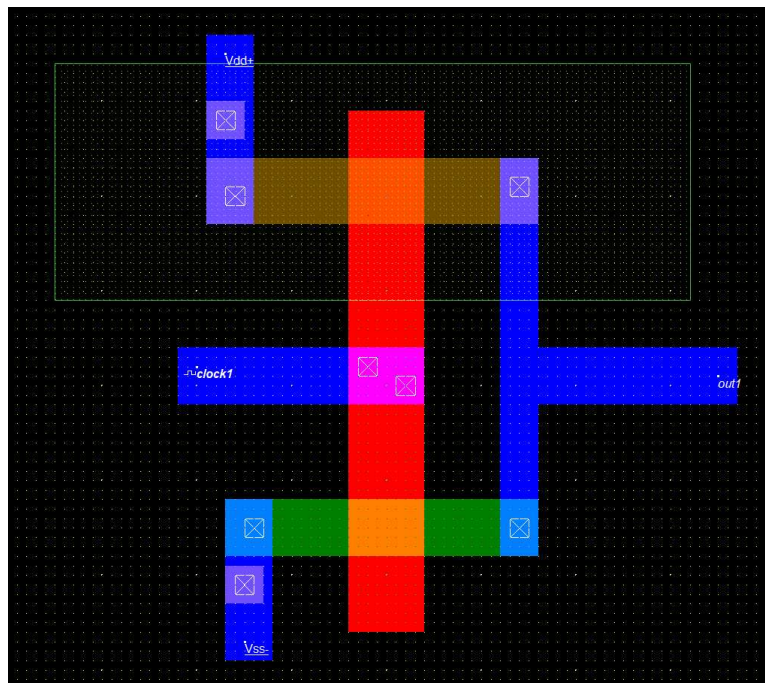


Rahul Bhadane


23104B0003

AVLSIDT LAB 3



CMOS INVERTER




Output:

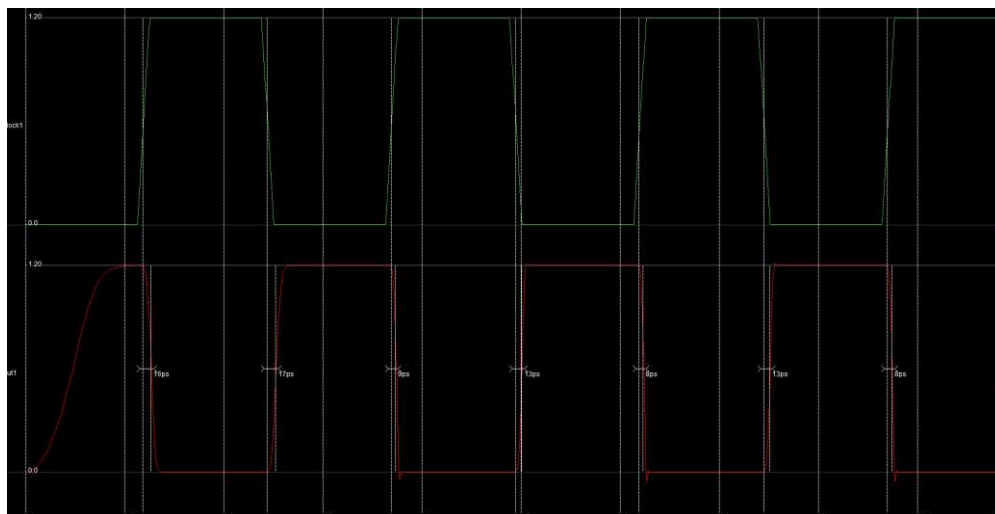

NAND GATE

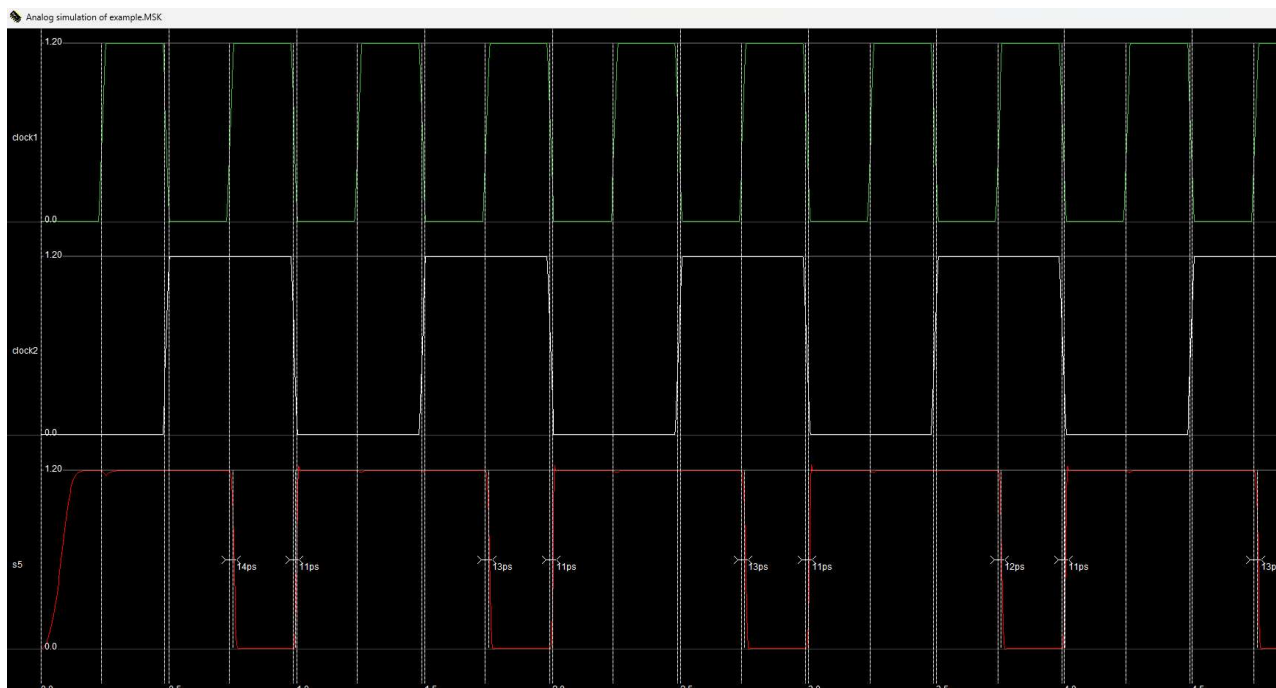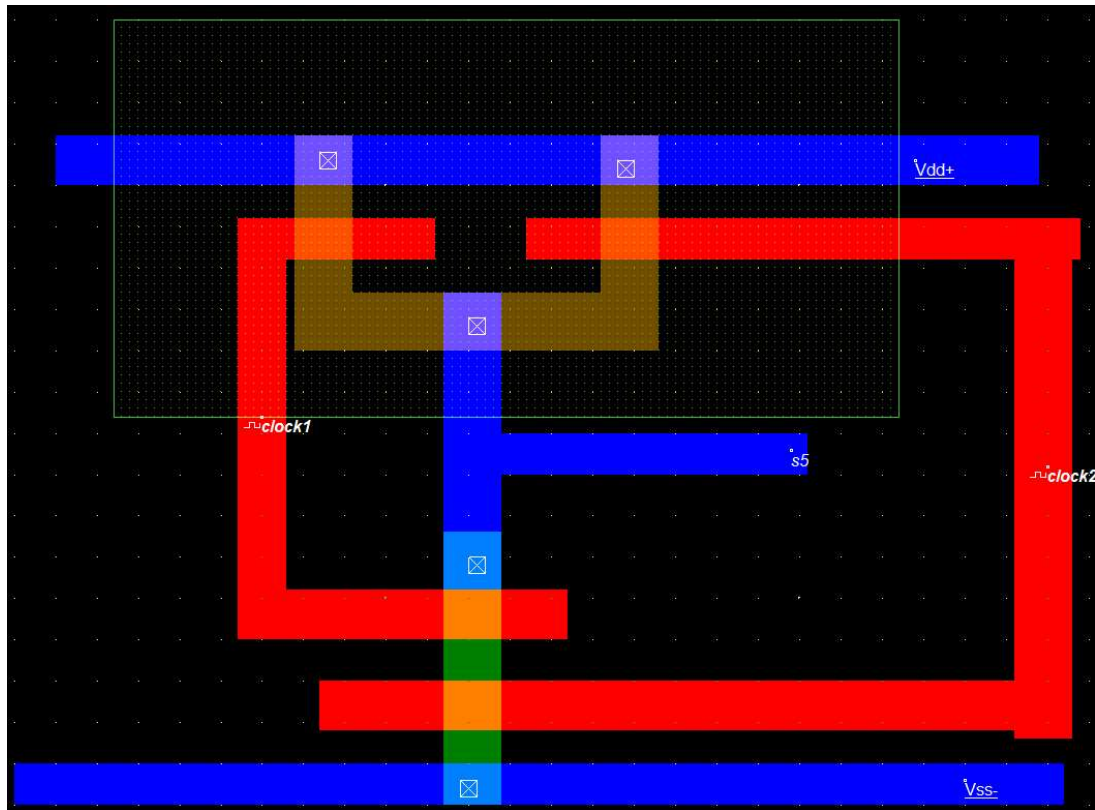

NOR GATE

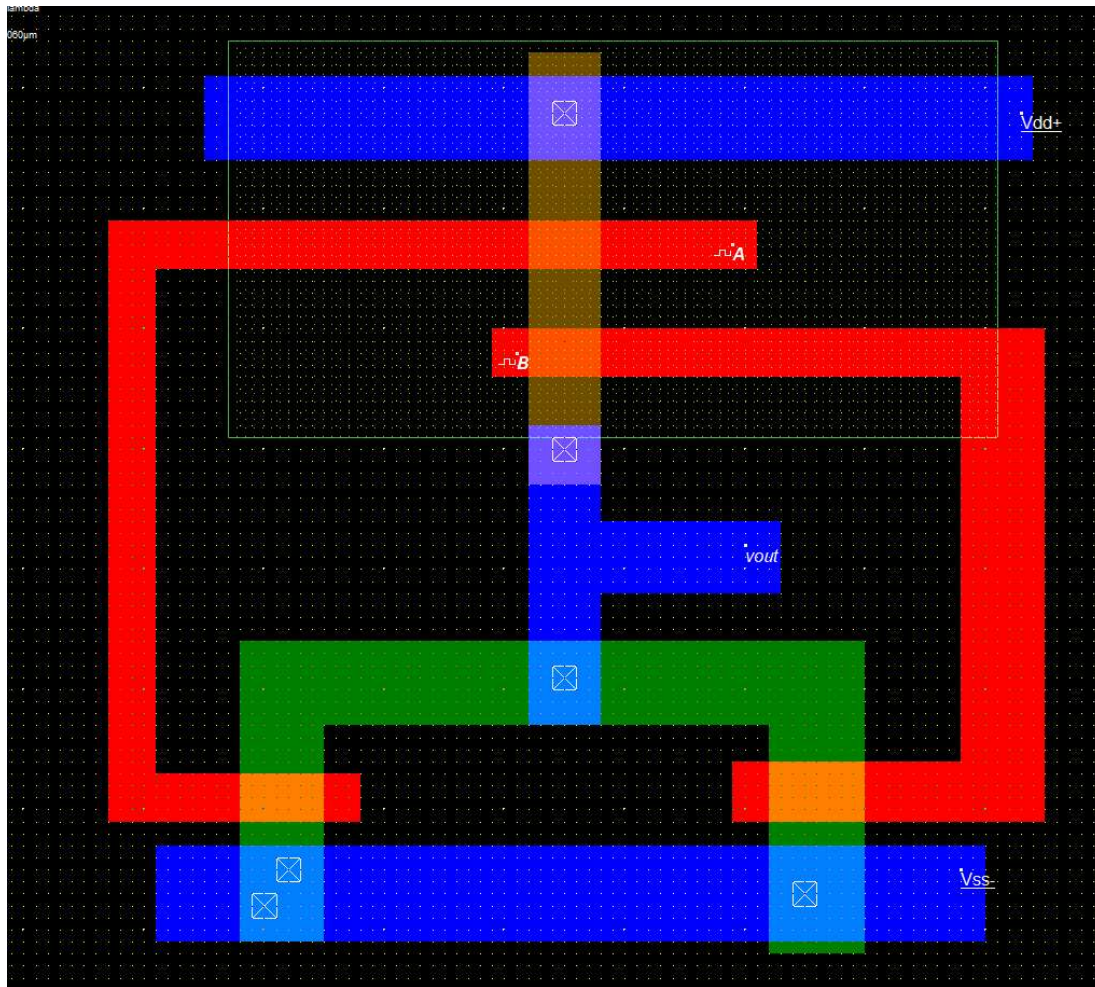

Output:

